


Quadrature Down Convertor

AEC Project | Spring2021

Mayank Shivhare
ECE, IIIT H

Ajay Ray
ECE, IIIT H

Tejas Srivastava
ECE, IIIT H

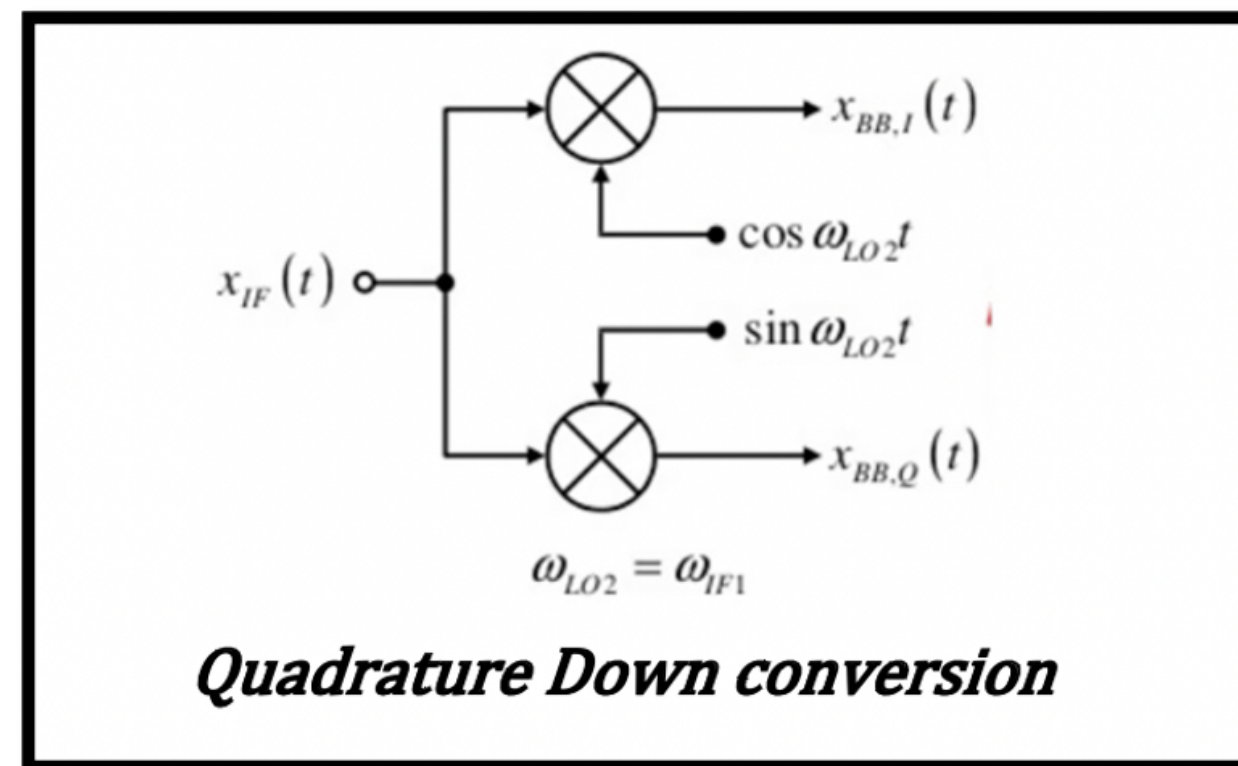

1 Quadrature Oscillator

Its function


It generates two sinusoidal signals of certain frequency with a phase difference of 90°

Circuit Diagram and Components

2 **UA741** OP-AMPs

Resistors



Capacitors

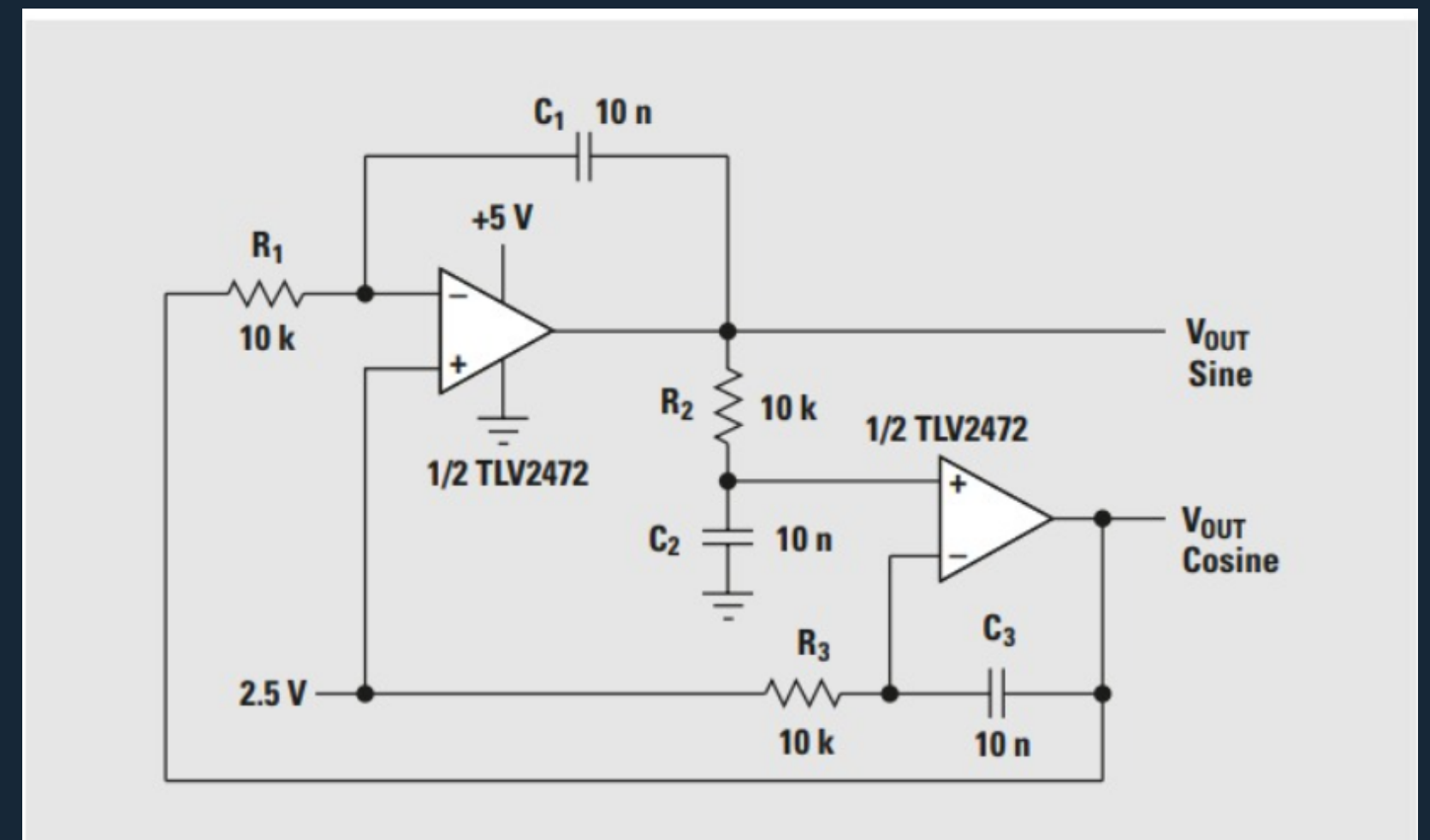

1 Quadrature Oscillator

LT-Spice Circuit

pindiagram of ua741

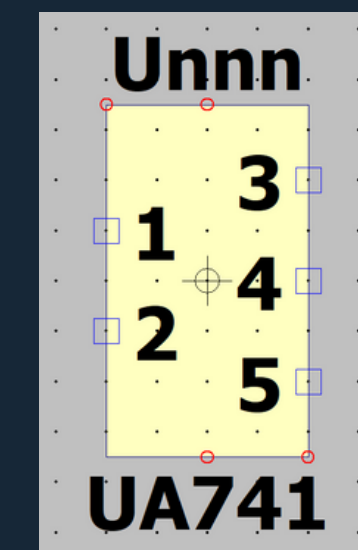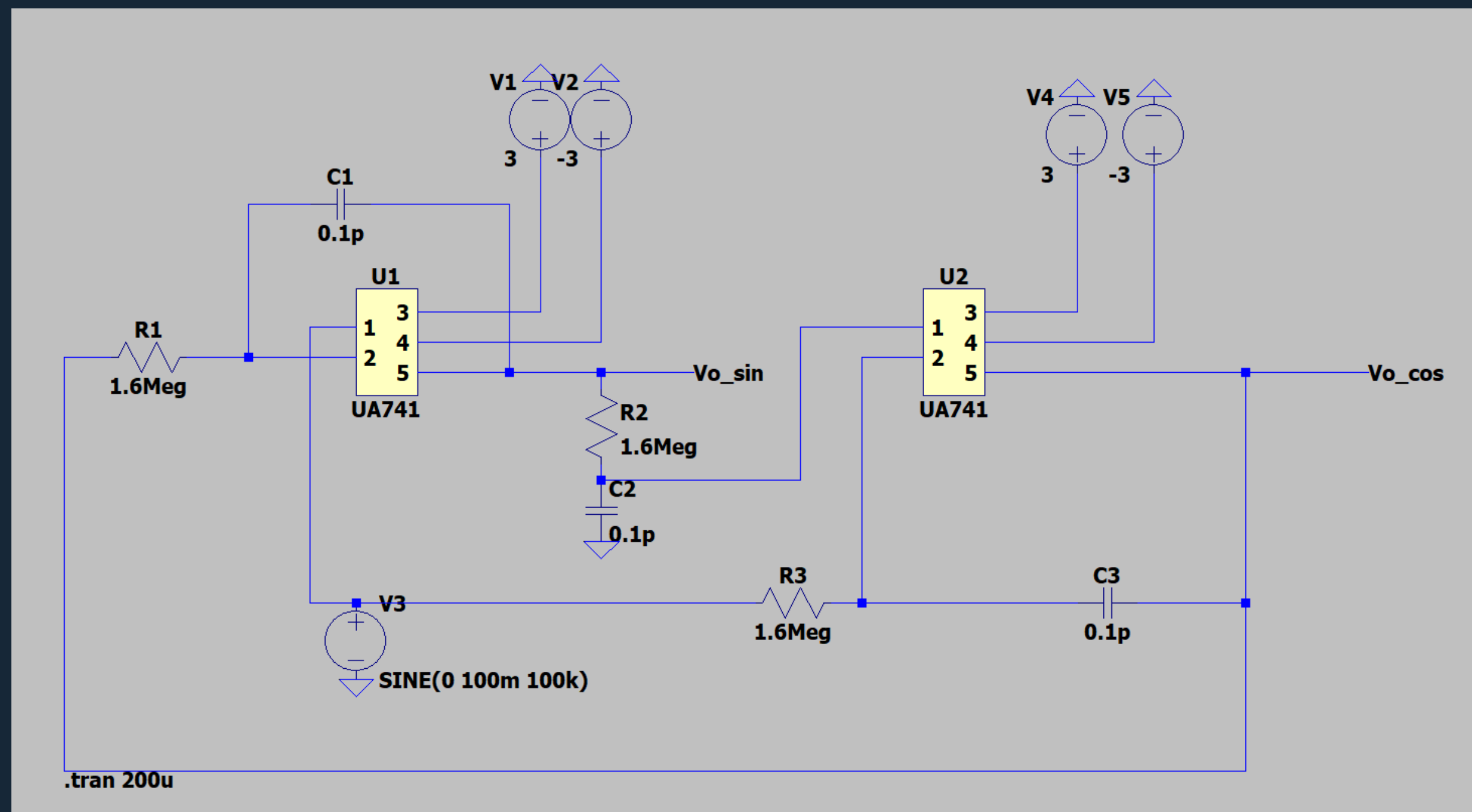


- 1 - V(+)
- 2 - V(-)
- 3 - Vdd
- 4 - Vss
- 5 - Vout

1

Quadrature Oscillator

LT-Spice Simulation Results

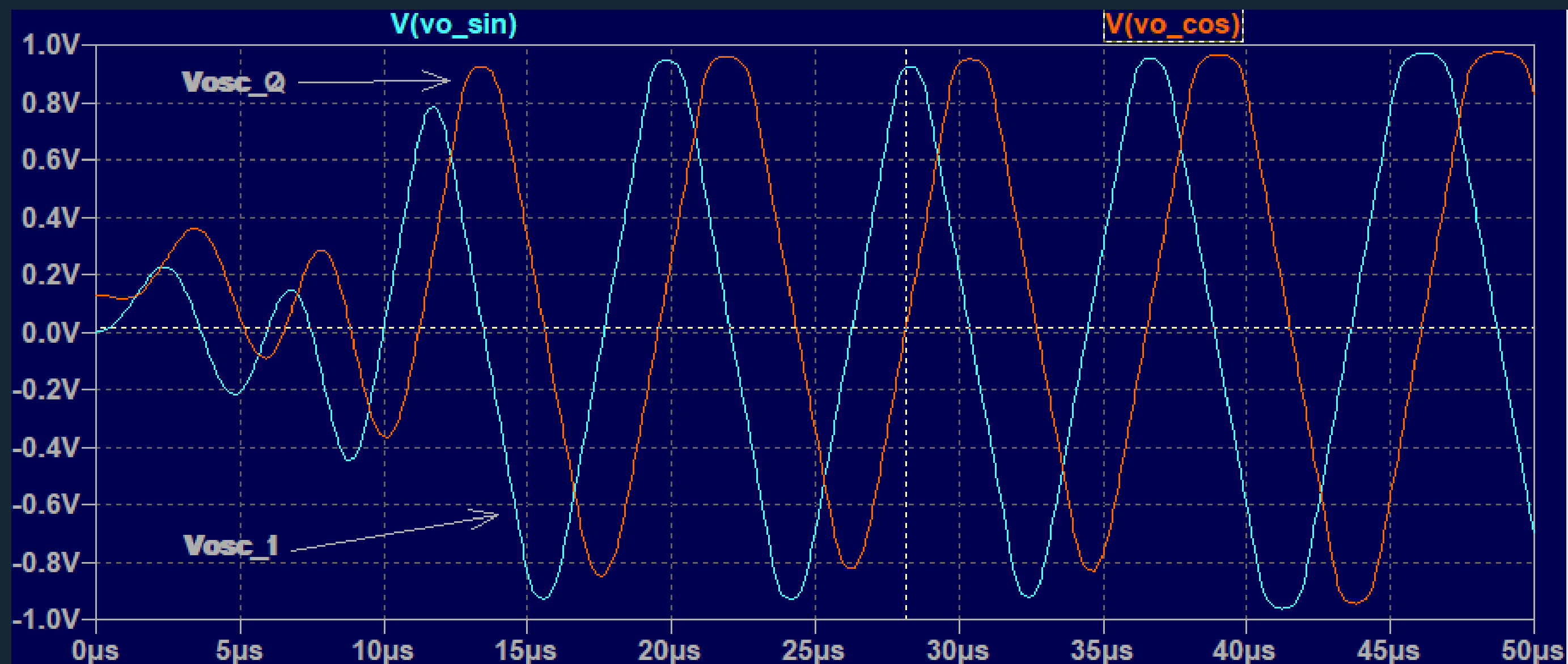


1

Quadrature Oscillator

LT-Spice Simulation Results

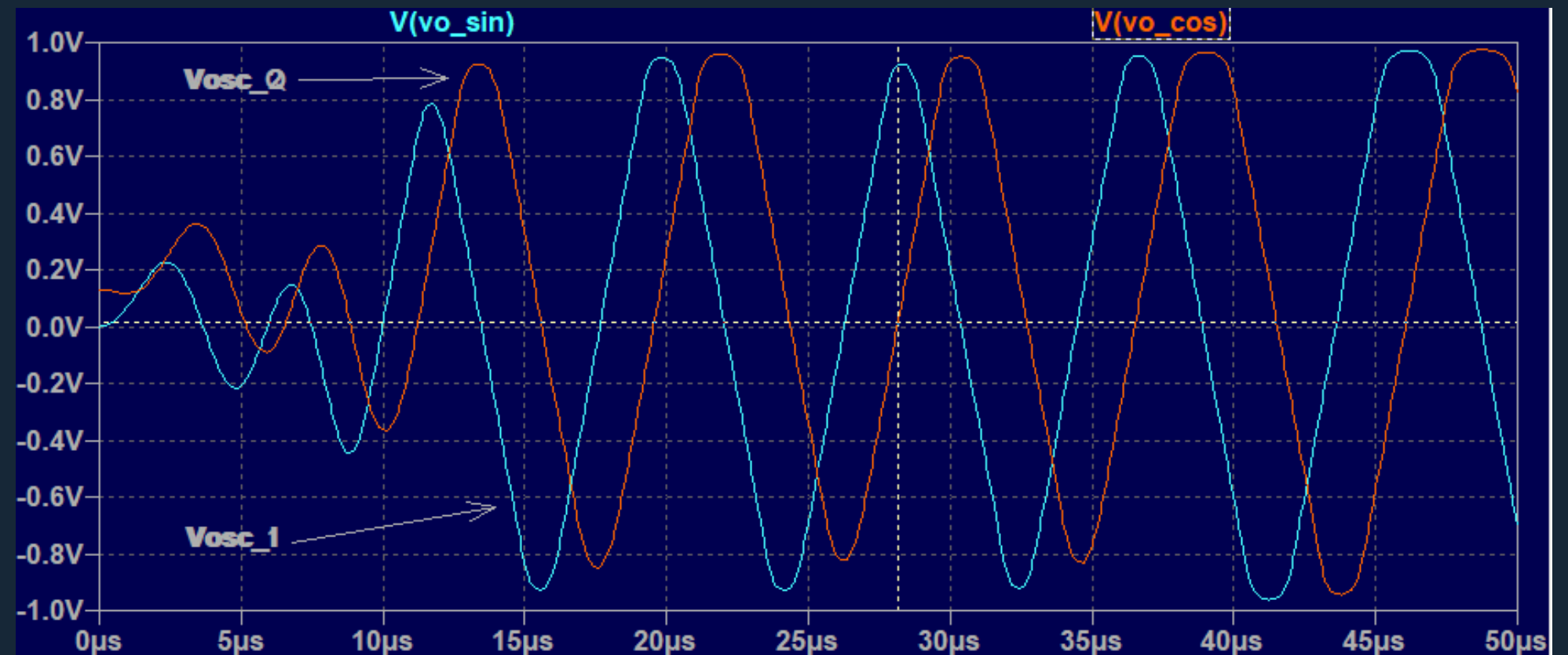- Only the noise signal is used to generate the outputs
- Amplitude of both the outputs are almost same ($\sim 0.9\text{V}$)
- Frequency is same as that of the noise signal
- Phase difference b/w the the two outputs is around 90°




2 Mixer Circuit (Switch Design)

Its function

It multiplies two sinusoidal input signals to give the output signal

Circuit Diagram and Components

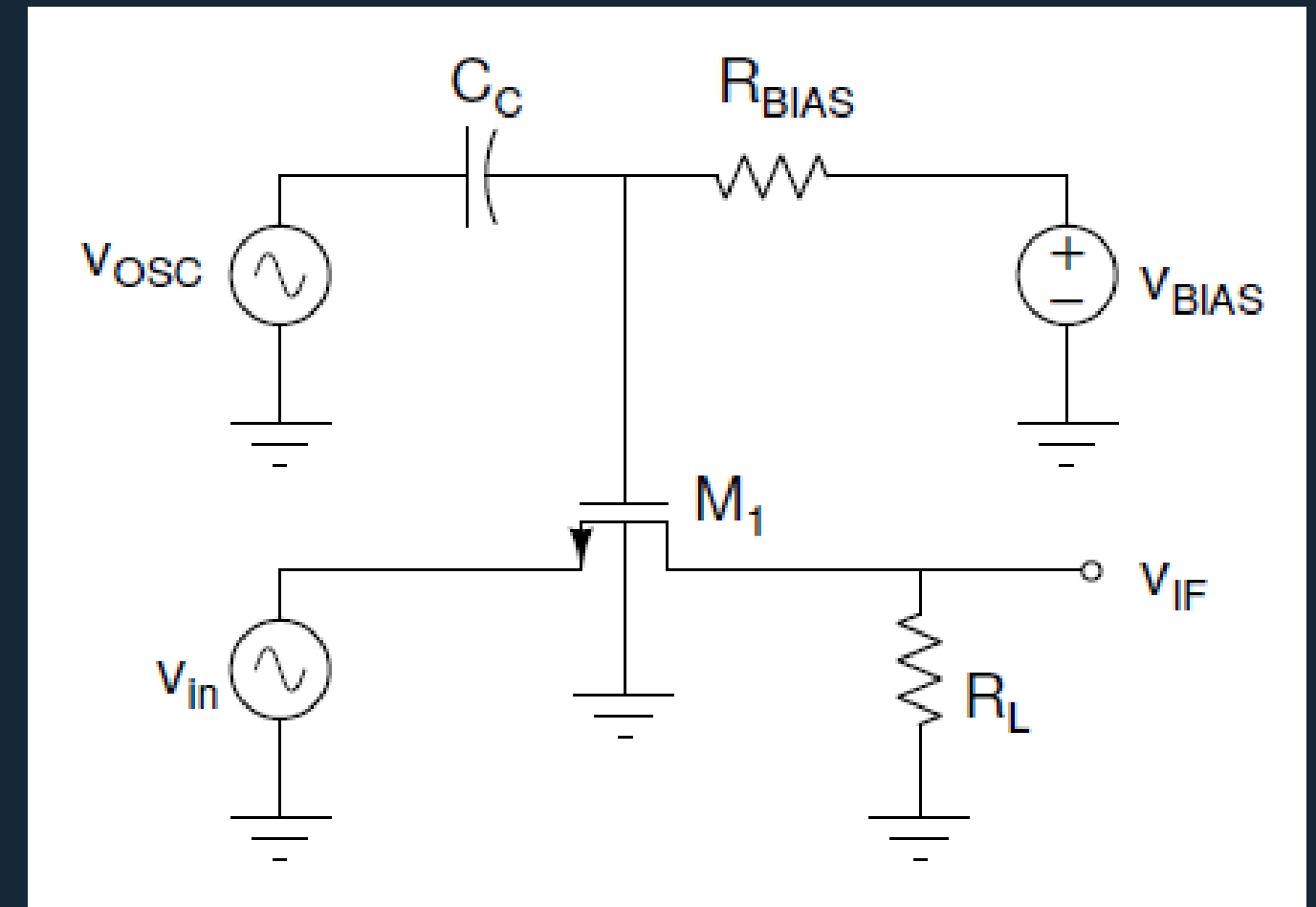
- **1 NMOS**
- Resistor R_C and bias resistor
- Capacitor C_C



2 Mixer Circuit (Switch Design)

Functioning

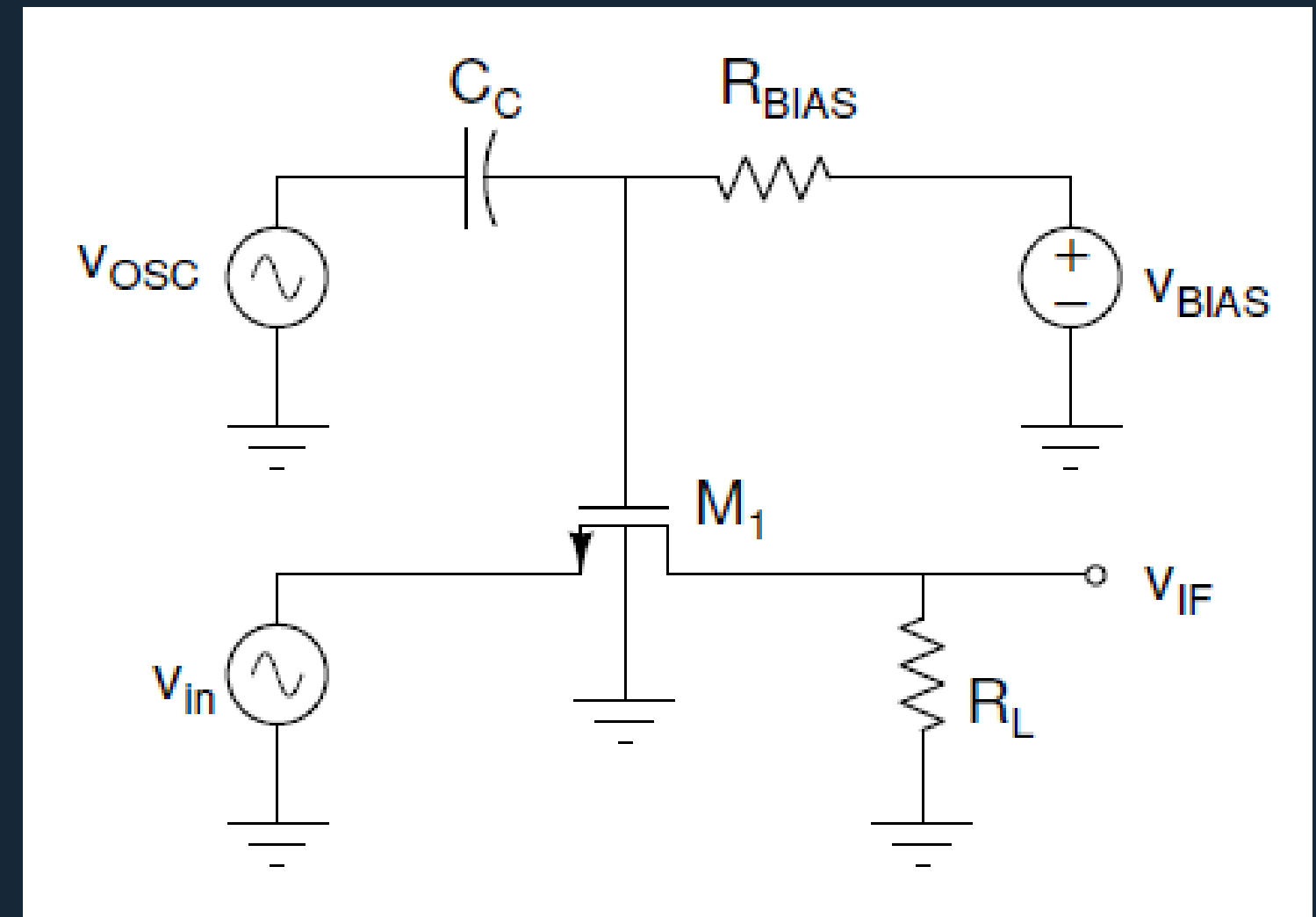
- V (bias) is given to be around $V(T)$ so that the circuit switches on and off as per the sinusoidal signal
- C_C blocks the AC component from V_{osc} in DC analysis
- $R(bias)$ blocks the DC component of $V(bias)$ from interfering in AC analysis



Circuit Diagram

2 Mixer Circuit (Switch Design)

LT-Spice Circuit

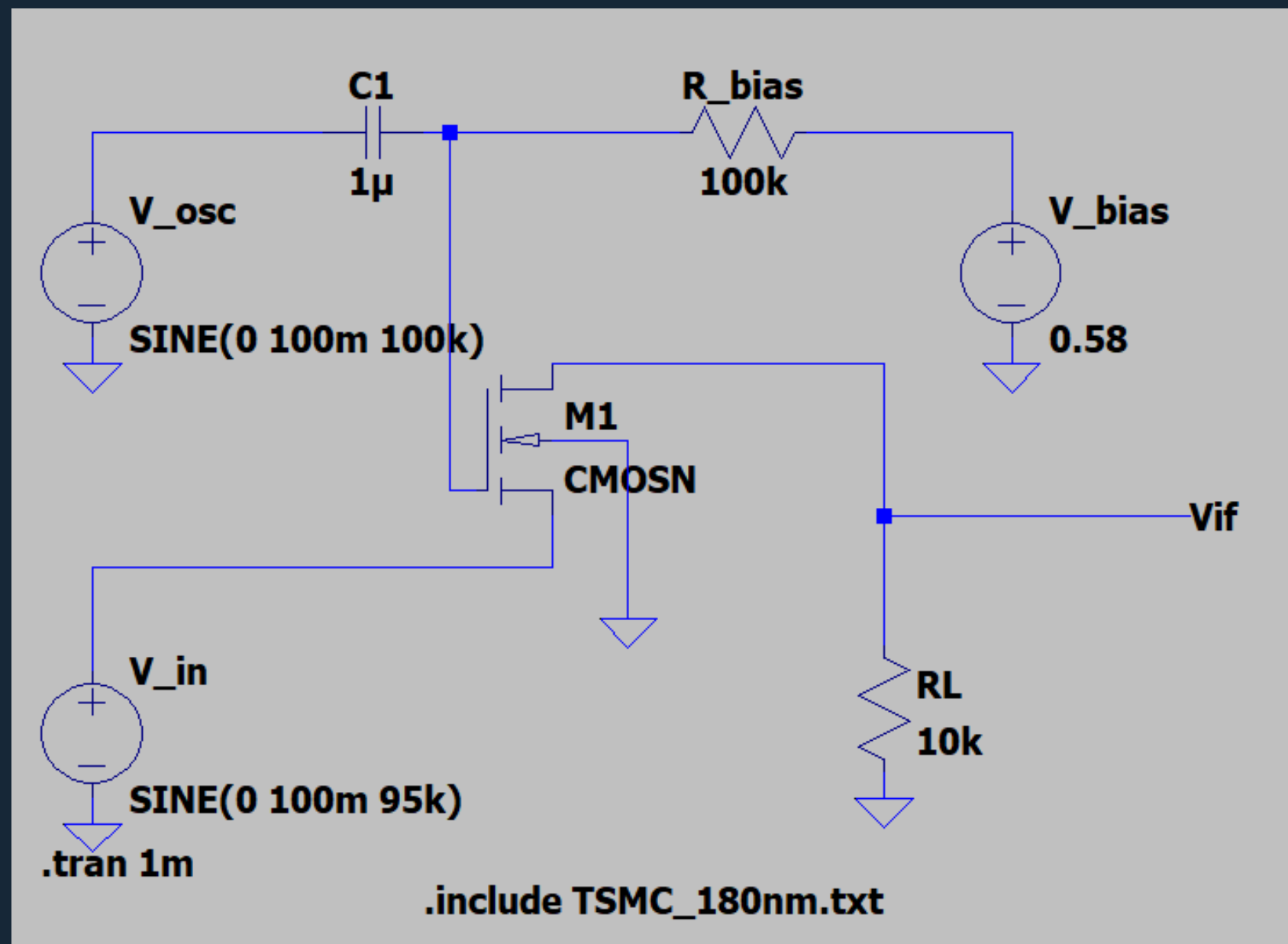

NMOS Parameters

Monolithic MOSFET - M1

Model Name:	CMOSN	OK
Length(L):	0.09u	Cancel
Width(W):	1.8u	
Drain Area(AD):	0.81p	
Source Area(AS):	0.81p	
Drain Perimeter(PD):	4.5u	
Source Perimeter(PS):	4.5u	
No. Parallel Devices(M):		

2 Mixer Circuit (Switch Design)


LT-Spice Simulations

$$V_{out} = V_{osc} \times V_{in}$$

- $R(\text{load}) = 10\text{k}\Omega$
- $C_c = 1\mu\text{F}$
- $R(\text{bias}) = 100\text{k}\Omega$

$$V_{in} = 0.1 \sin(2\pi f_1 t)$$

$$V_{osc} = 0.1 \sin(2\pi f_2 t)$$

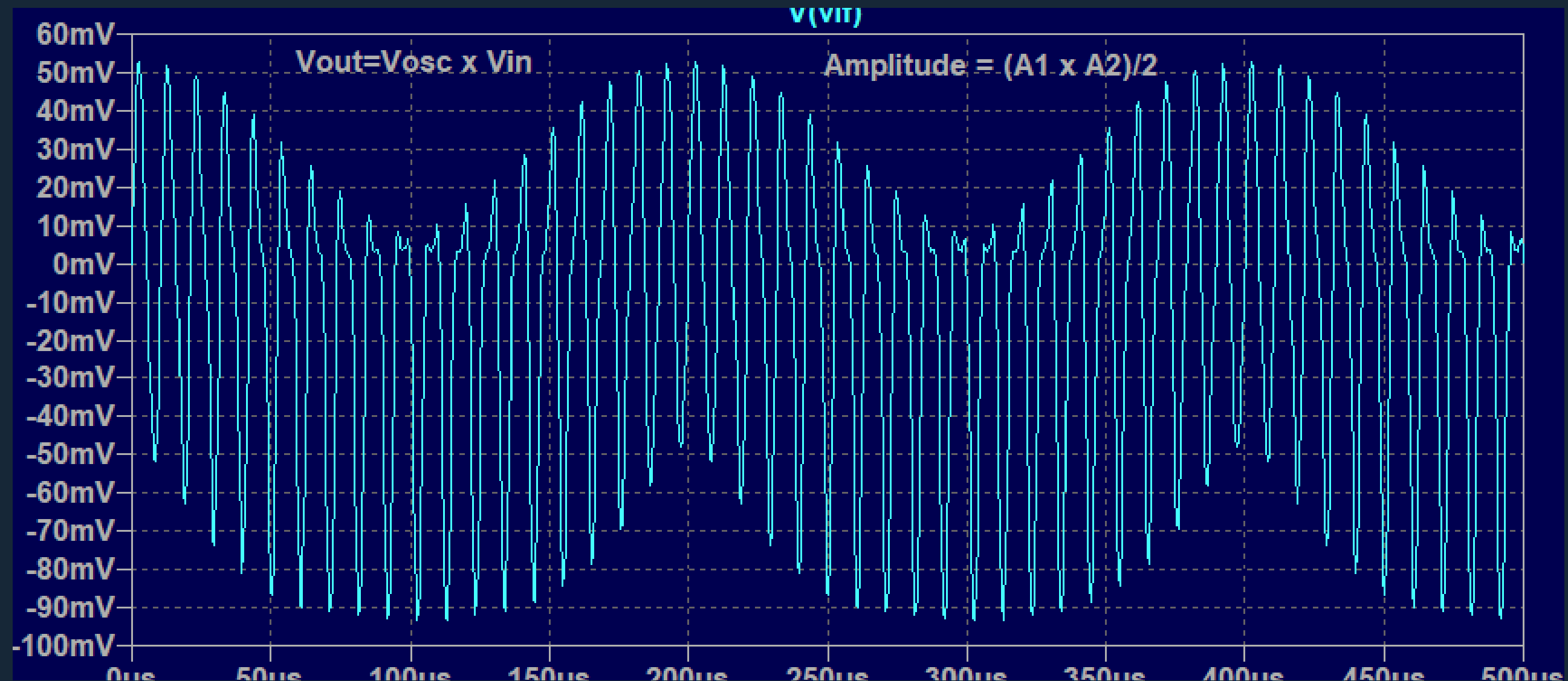


2 Mixer Circuit (Switch Design)


LT-Spice Simulations

$$v_{IF_I} = v_{in} \times v_{OSC_I} = \frac{A_1 A_2}{2} (\cos(\omega_{in} t - \omega_{OSC} t) + \cos(\omega_{in} t + \omega_{OSC} t))$$
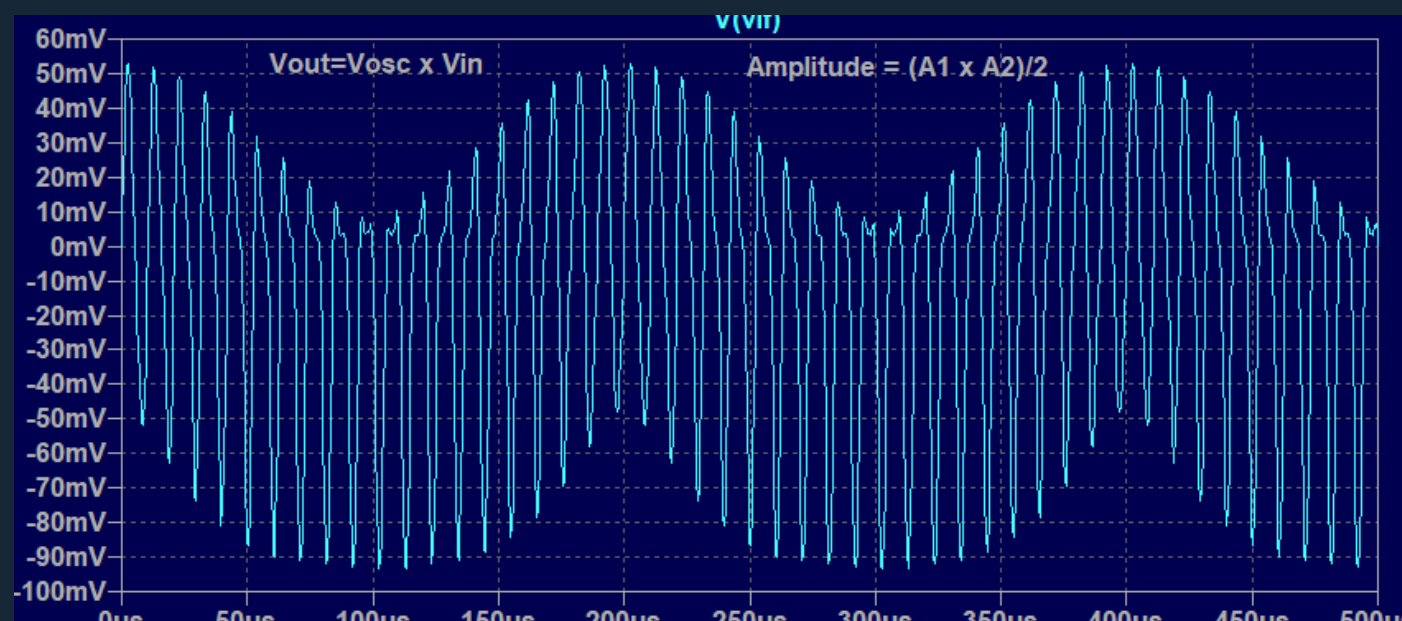
$$v_{IF_Q} = v_{in} \times v_{OSC_Q} = \frac{A_1 A_2}{2} (\sin(\omega_{in} t + \omega_{OSC} t) - \sin(\omega_{in} t - \omega_{OSC} t))$$




Obtained Waveform

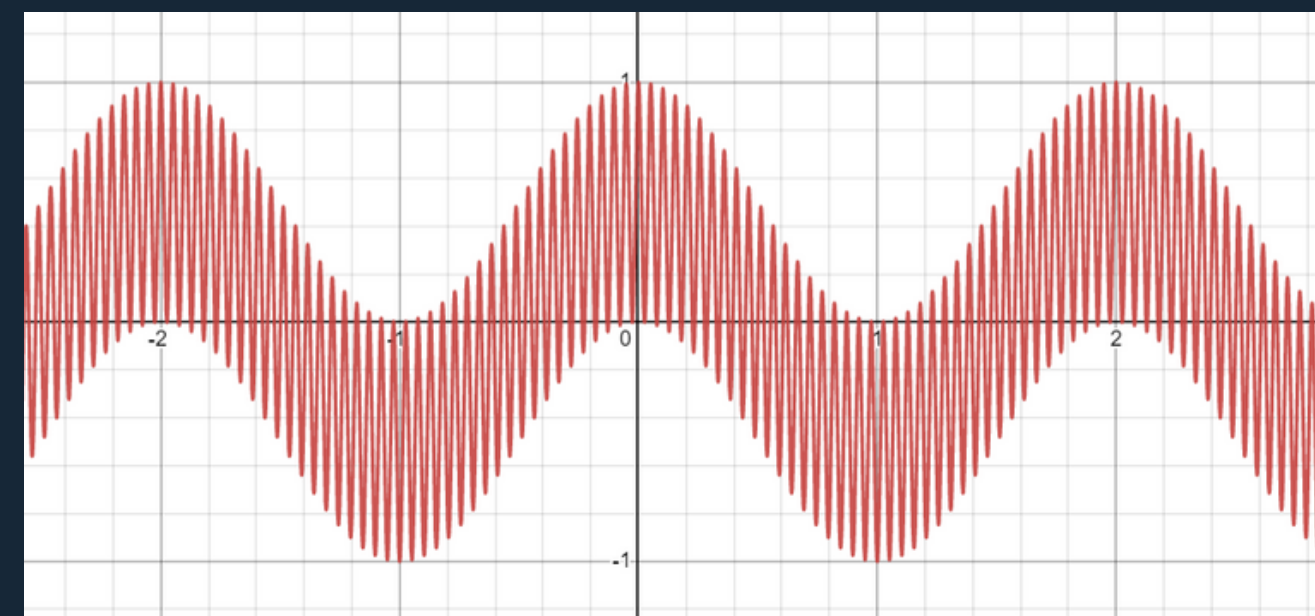


Theoretical Waveform

2 Mixer Circuit (Switch Design)

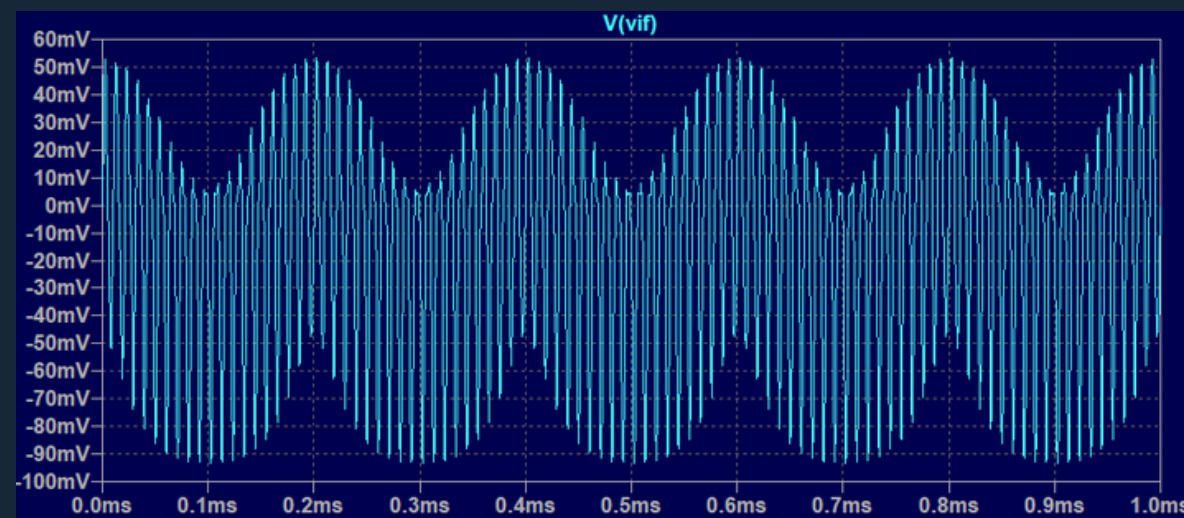
LT-Spice Simulations for various frequencies




$f_{in} = 95\text{kHz}$

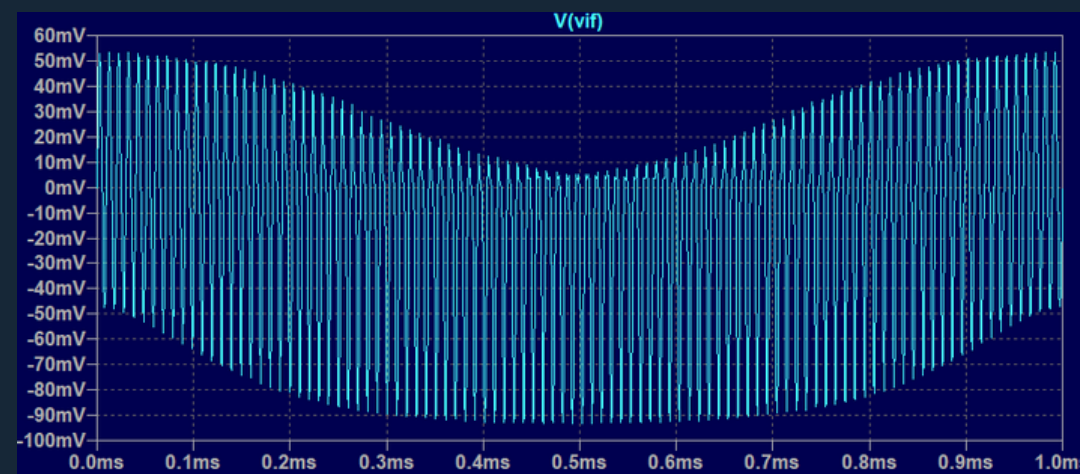


$f_{in} = 98\text{kHz}$

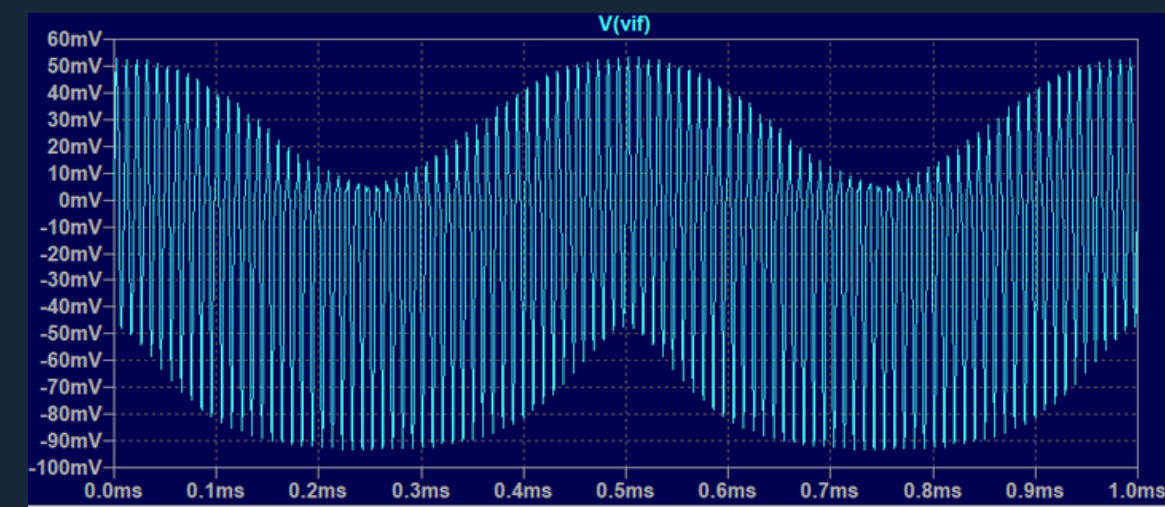


$f_{in} = 99\text{kHz}$

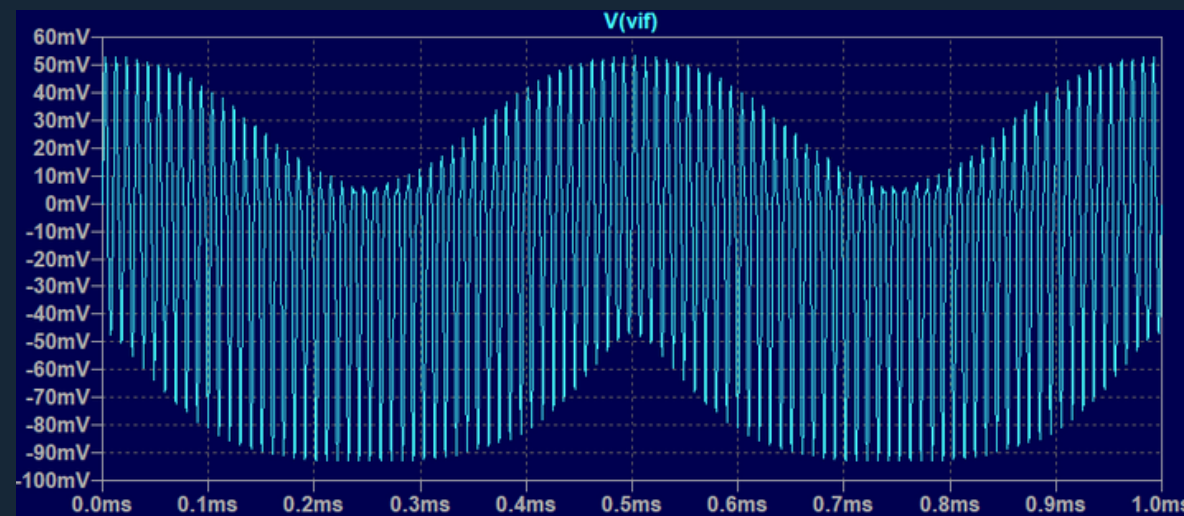

$f_{in} = 101\text{kHz}$

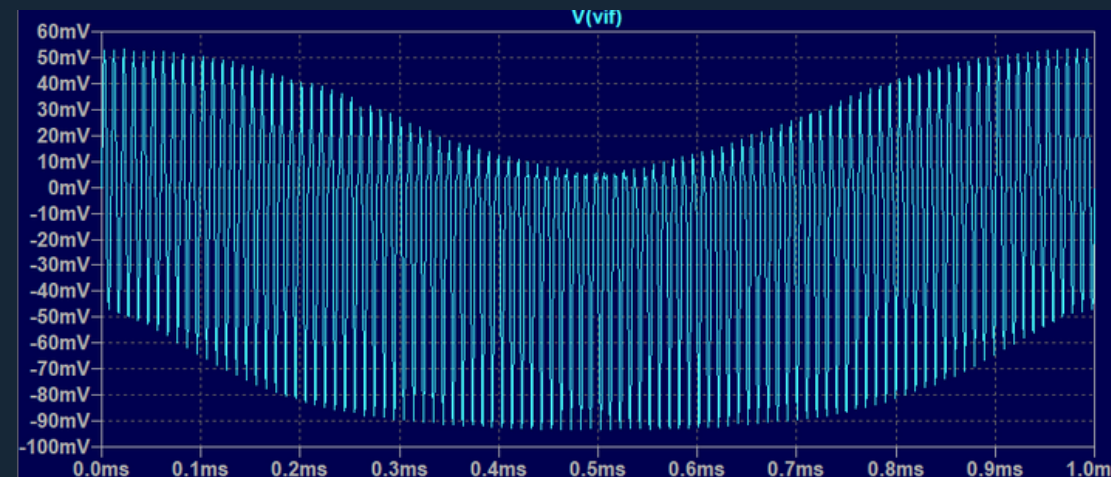


$f_{in} = 102\text{kHz}$

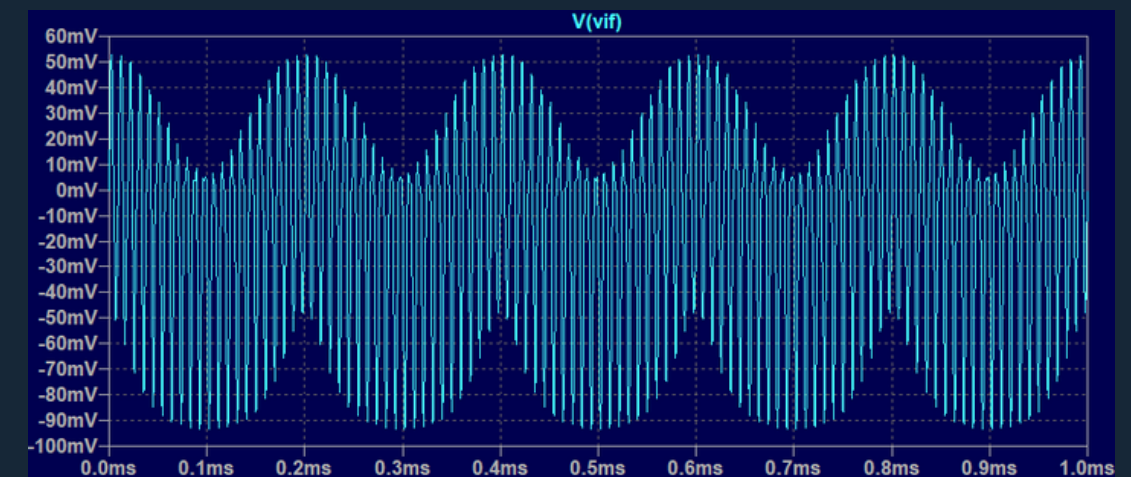

$f_{in} = 105\text{kHz}$

2 Mixer Circuit (Switch Design)

LT-Spice Simulations for FFT

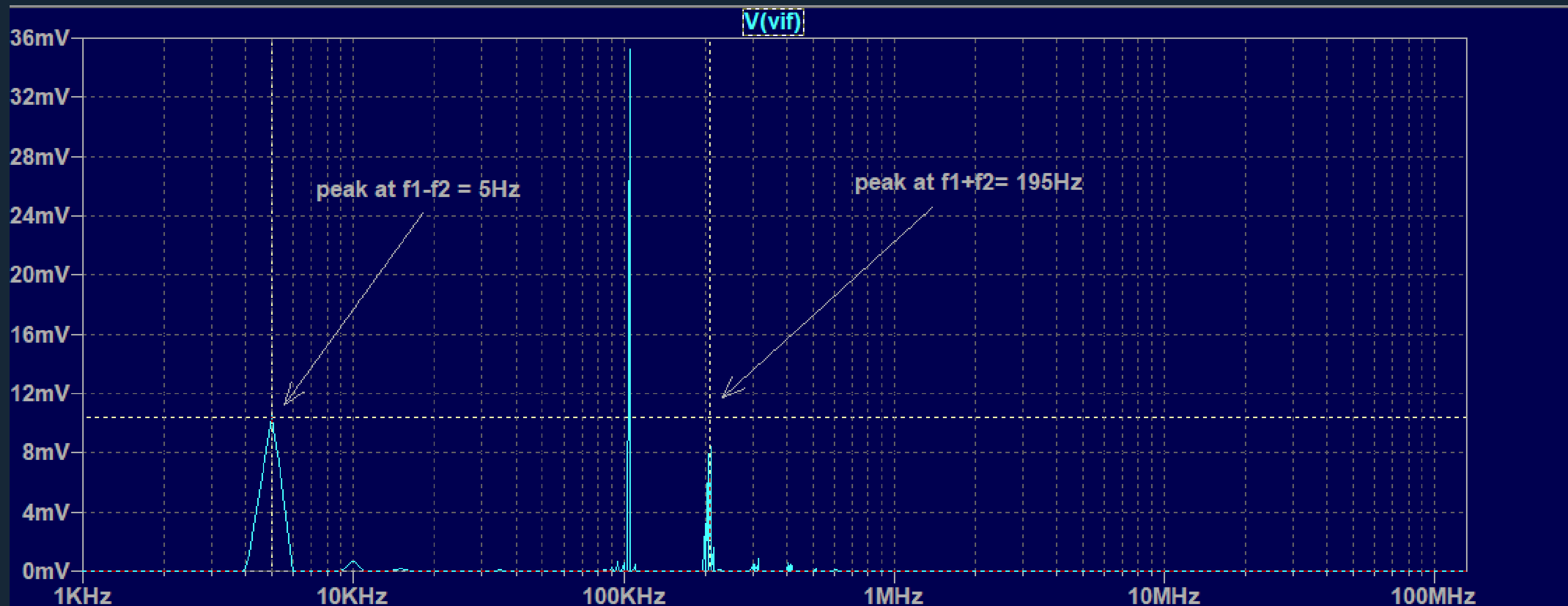

3 Low-Pass Filter

Its function


It filters out the high frequency components of the input signal based on value of RC

Circuit Diagram and Components

- Resistor $R = 16.5 \Omega$
- Capacitor $C = 4.7\mu\text{F}$

$$\text{-3dB frequency} = 1 / (2\pi RC) = 2\text{kHz}$$

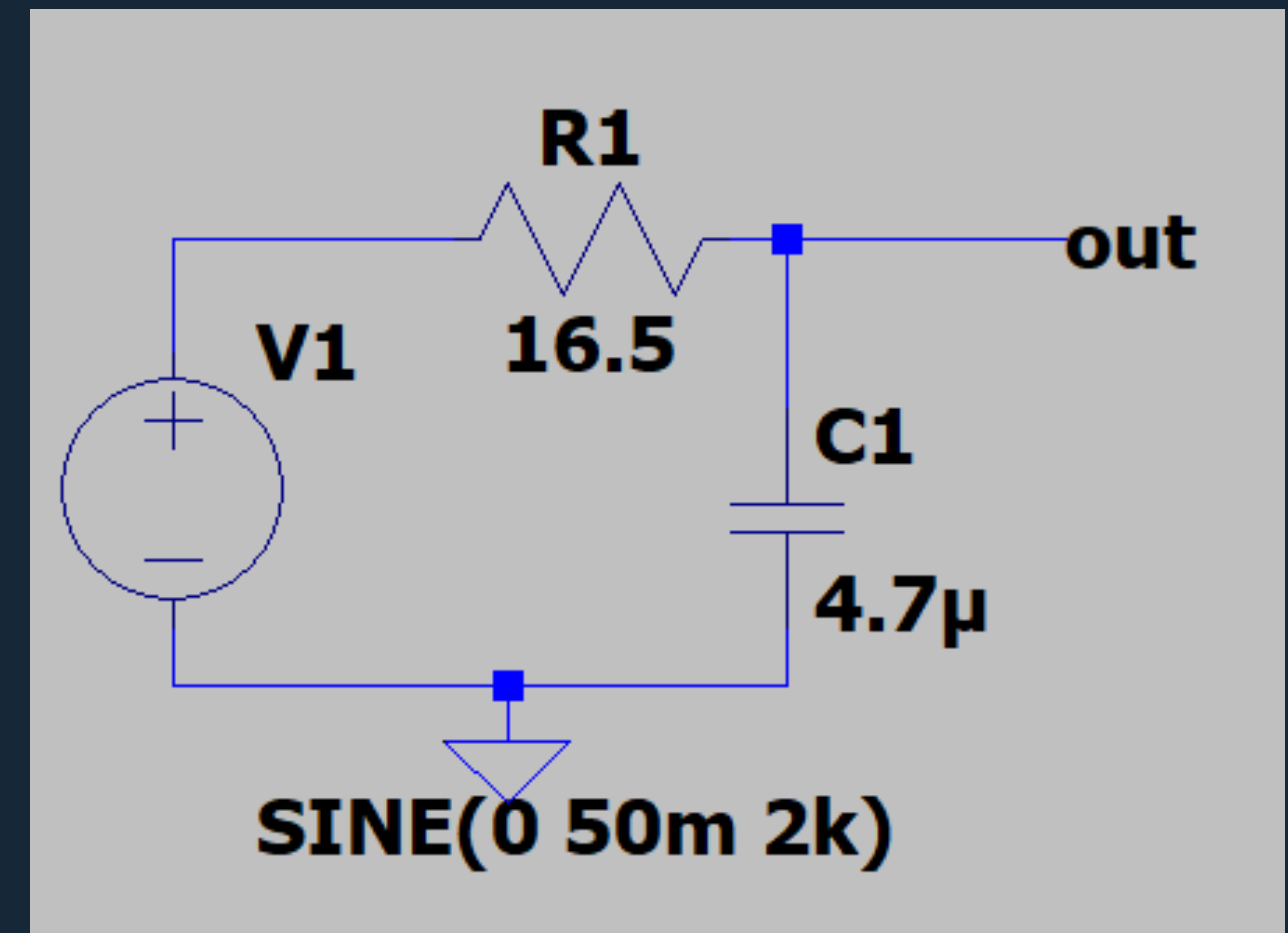
$$\text{cutoff} = 1 / (2\pi RC) = 1000000/487 = 2.053 \text{ kHz}$$




3 Low-Pass Filter

(Bode-Plot for RC Low Pass filter)

LT-Spice Simulations

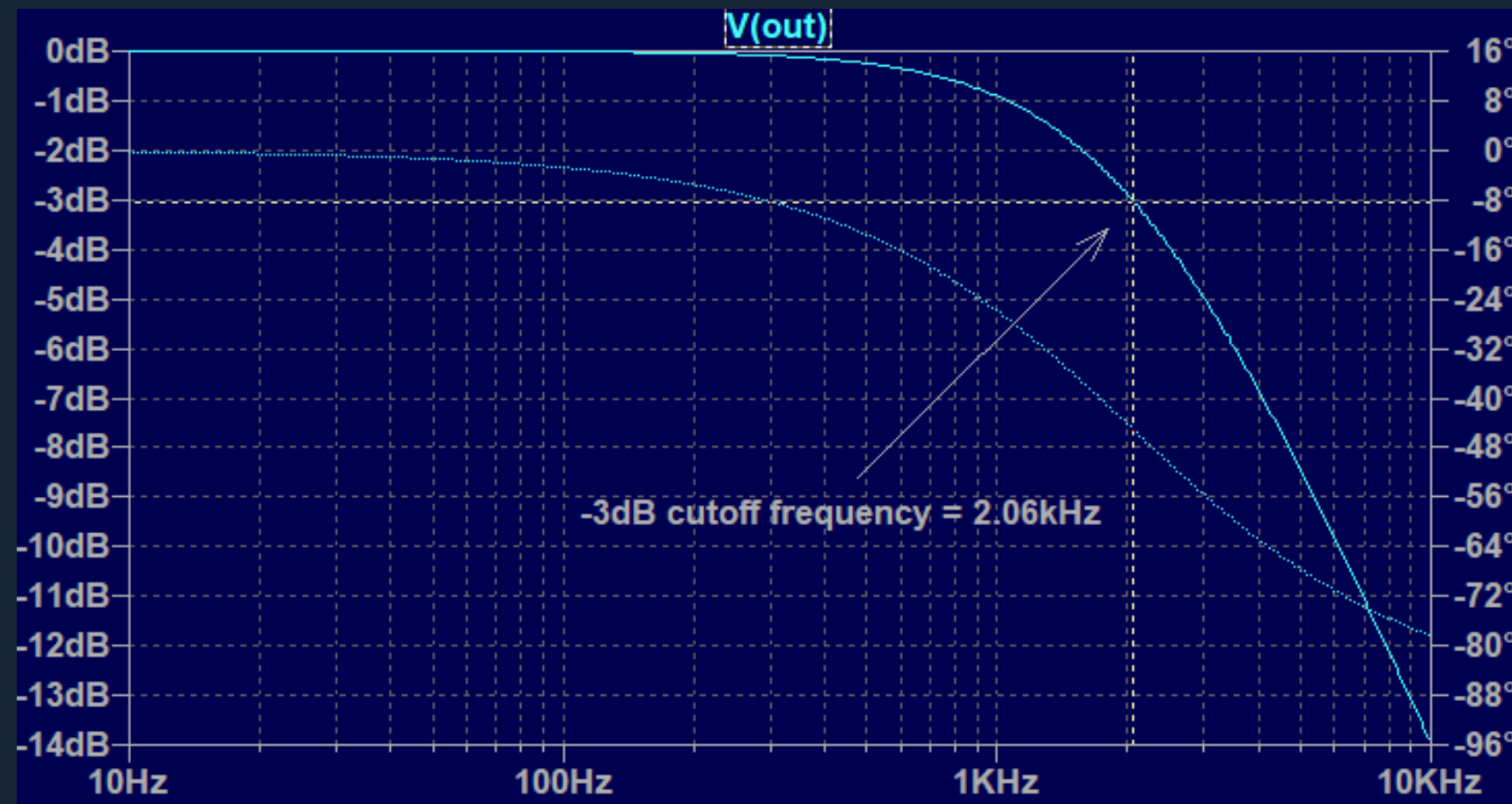


DSO output

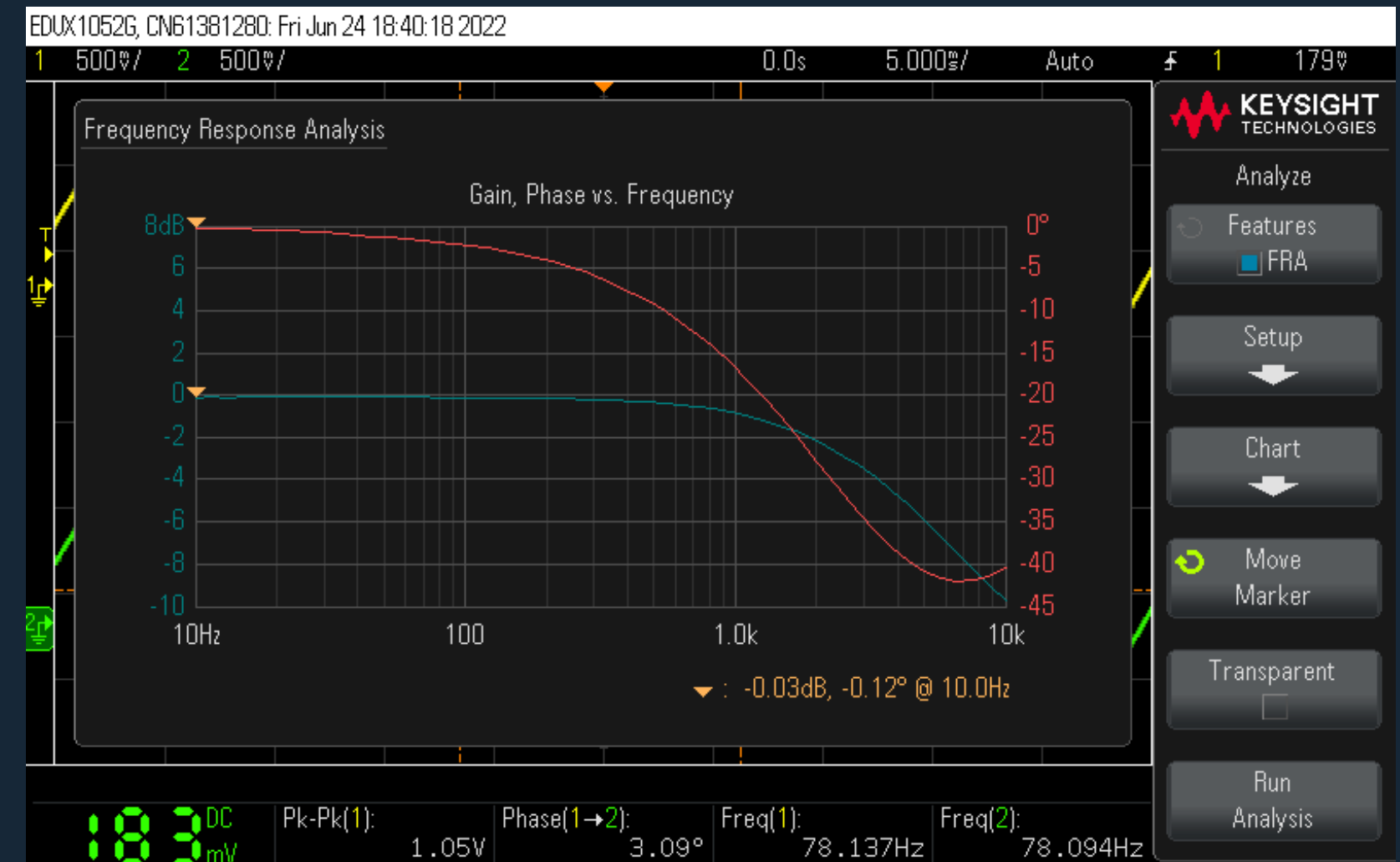


3 Low-Pass Filter

LT-Spice Simulations

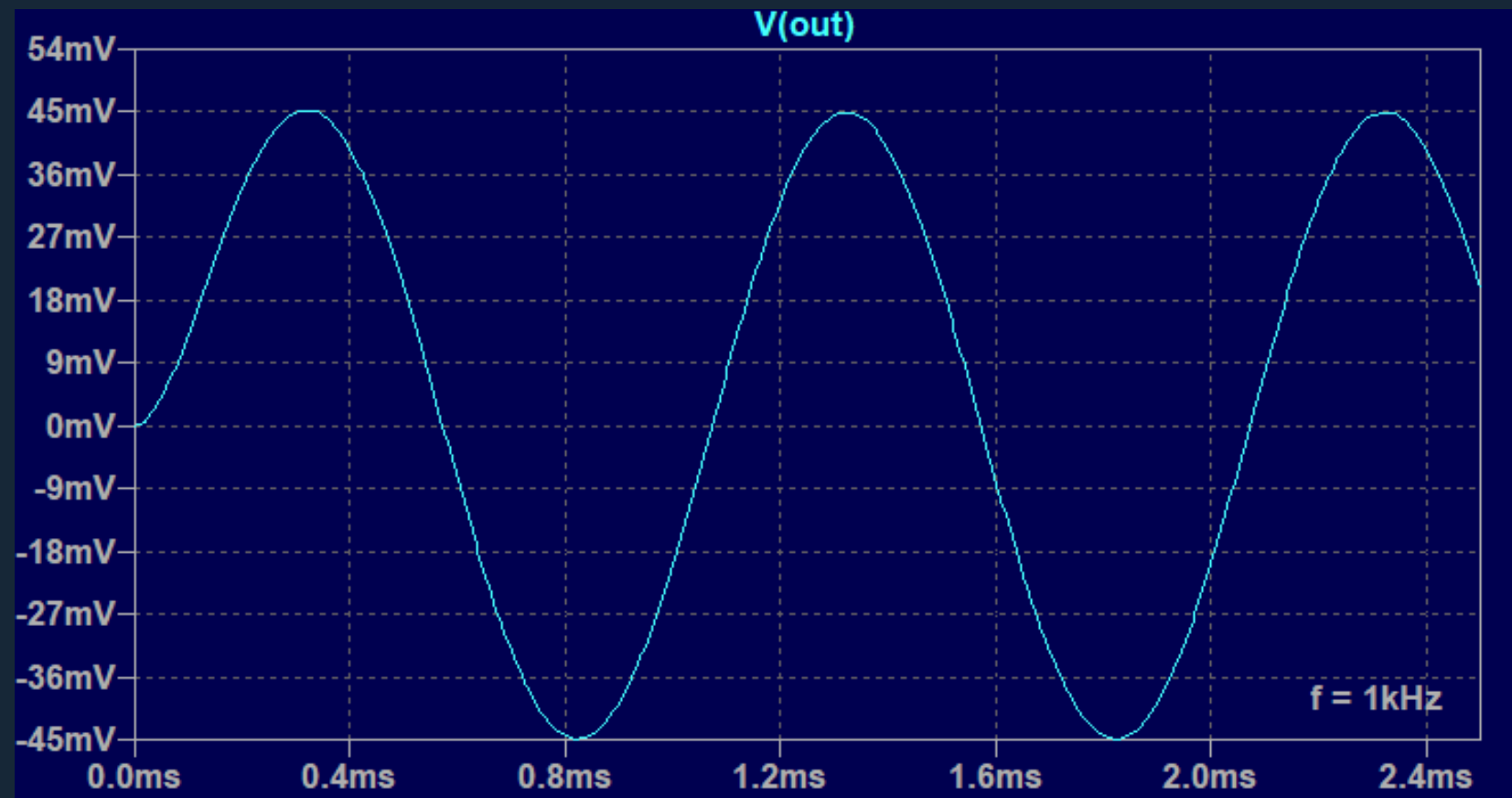

$V_{pp} = 90\text{mV}$

DSO output

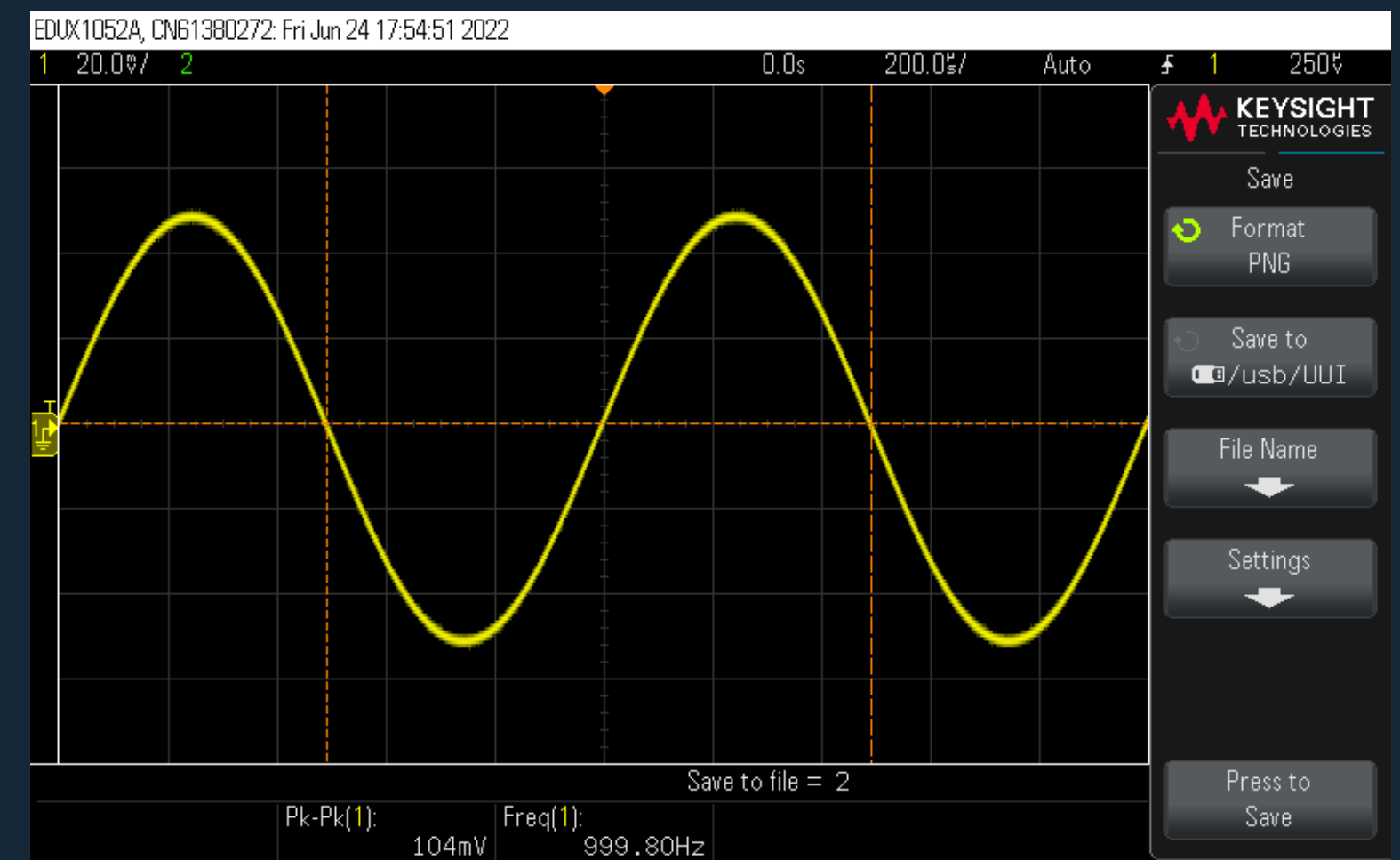


$V_{pp} = 104\text{mV}$

(Transient Response $V_{pp} = 100\text{mV}$ $f = 1\text{kHz}$)


3 Low-Pass Filter

LT-Spice Simulations

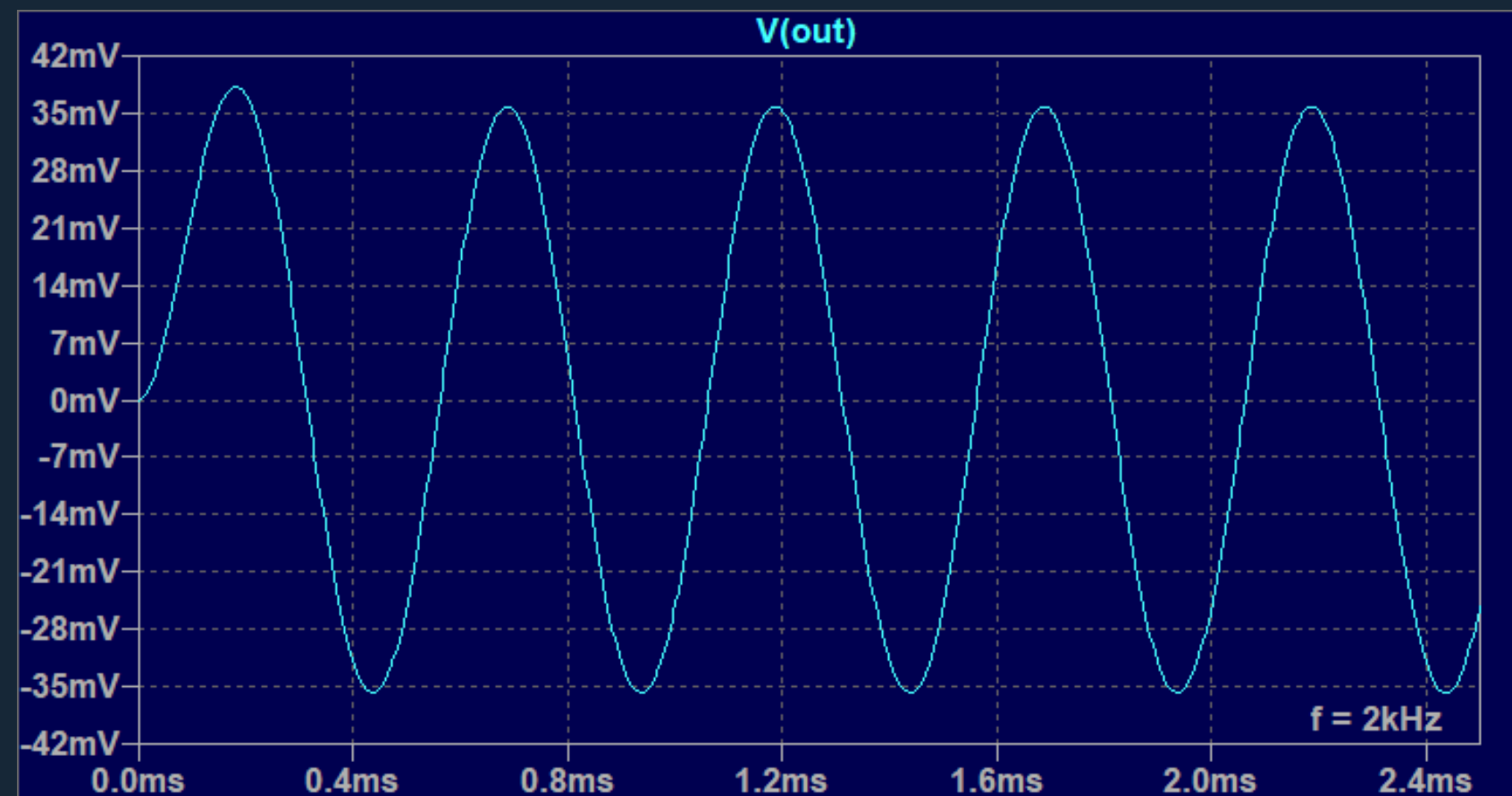

$$V_{pp} = 71\text{mV}$$

DSO output

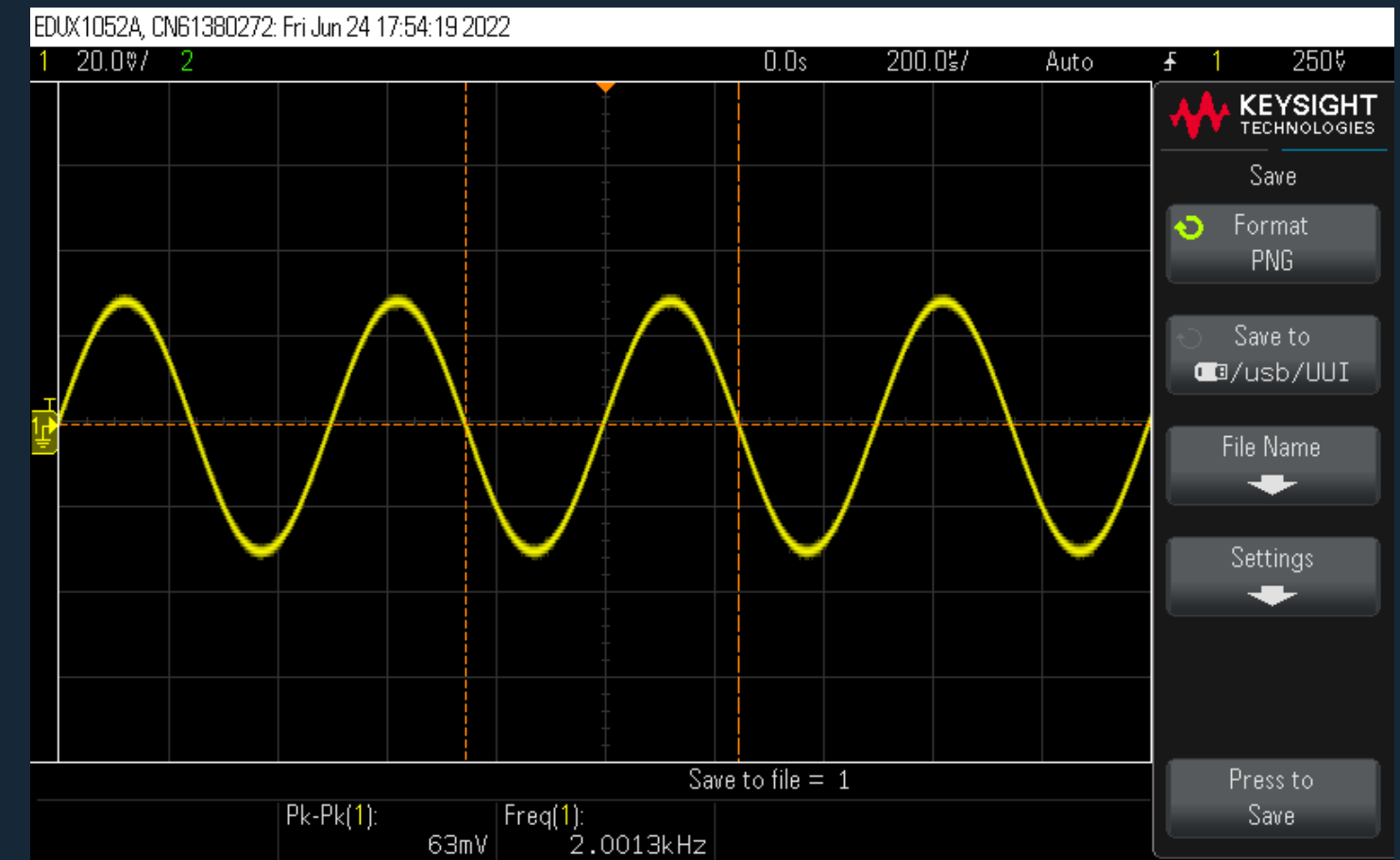


$$V_{pp} = 63\text{mV}$$

(Transient Response $V_{pp} = 100\text{mV}$ $f = 2\text{kHz}$)


3 Low-Pass Filter

LT-Spice Simulations

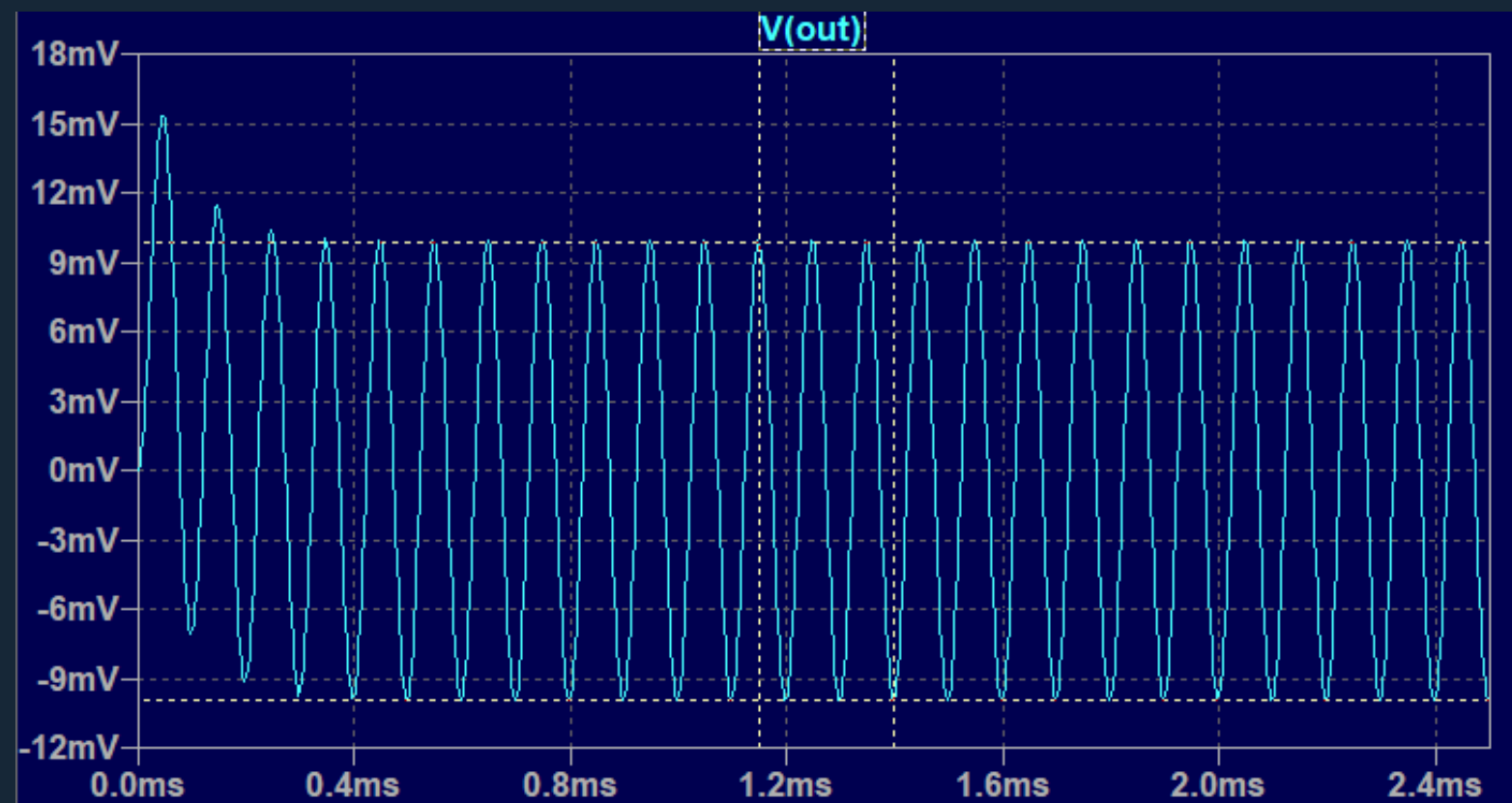

$$V_{pp} = 20\text{mV}$$

DSO output

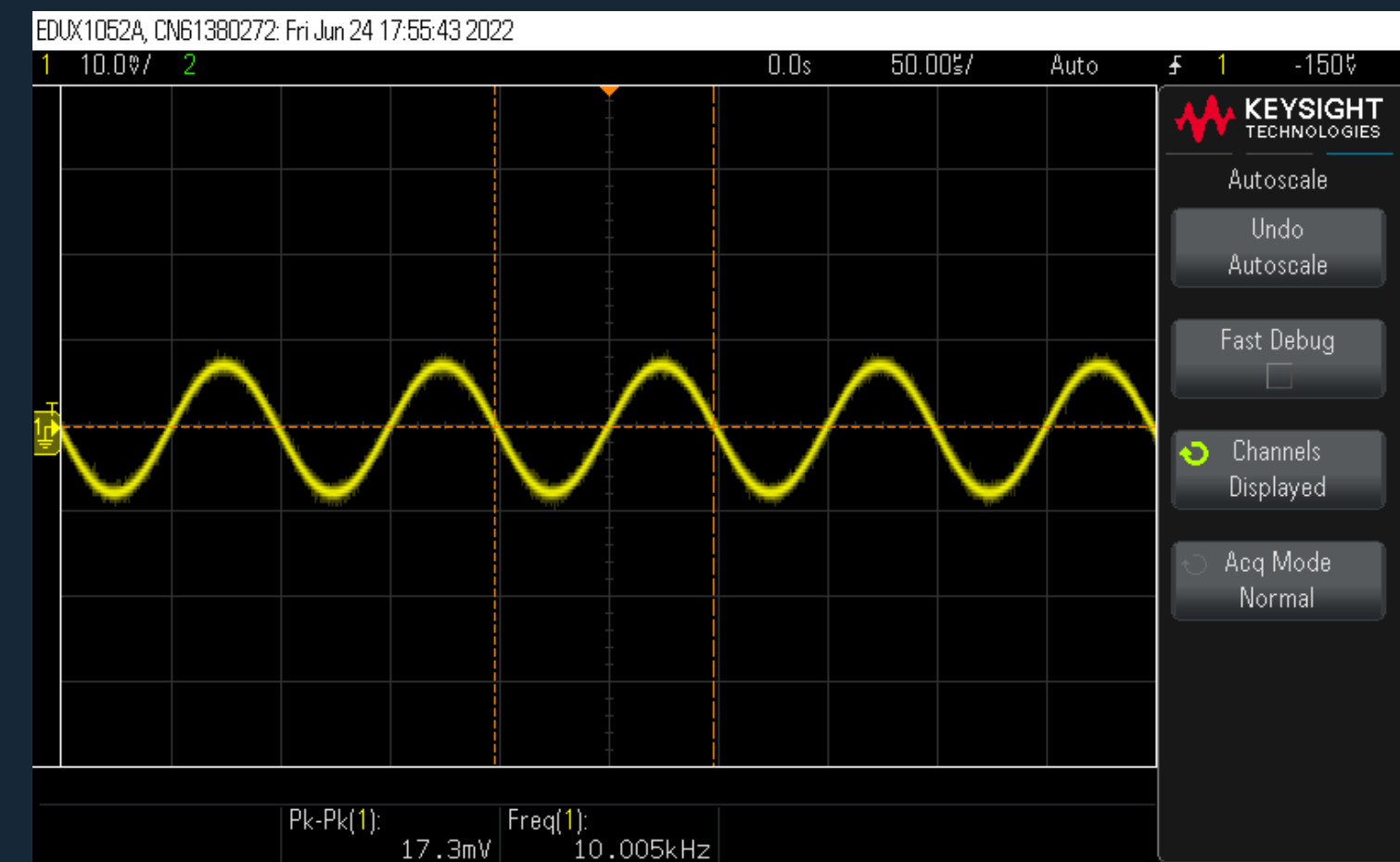

$$V_{pp} = 17\text{mV}$$

(Transient Response $V_{pp} = 100\text{mV}$ $f = 10\text{kHz}$)

Thankyou